


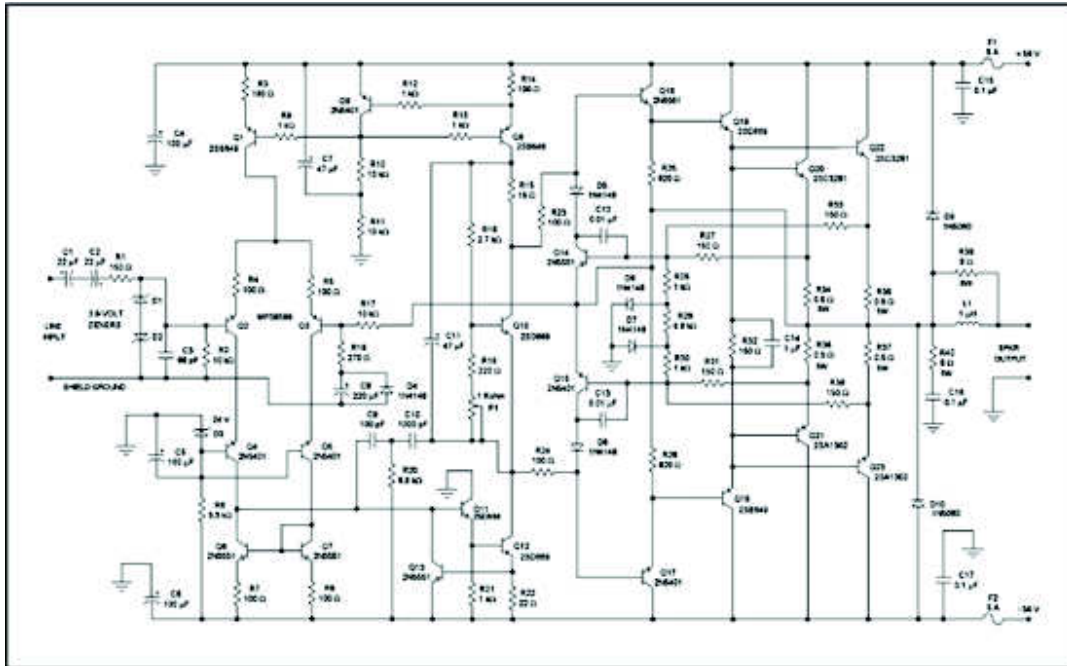


FIGURE 6.15 My favorite BJT audio power amplifier design.

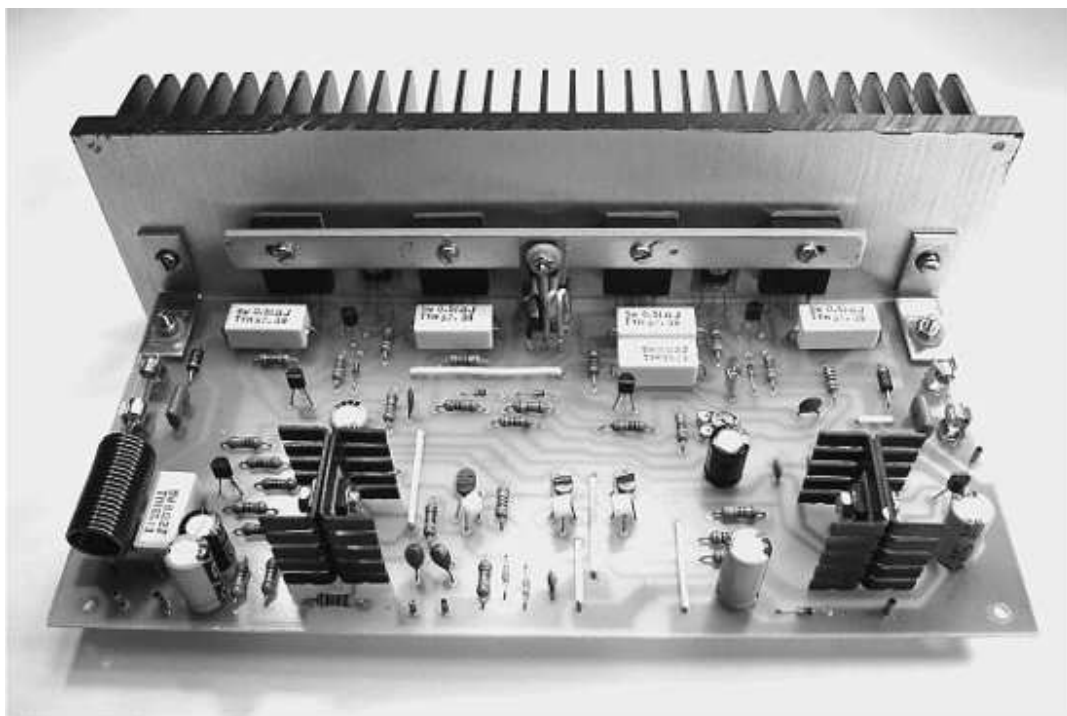

The completed [Fig. 6-15](#) audio power amplifier. Note the thermal bar mounted to the front surface of the output transistors, with the bias